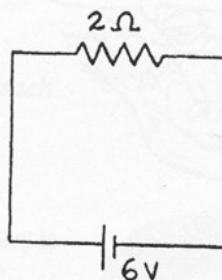



CONCEPTUAL Physics PRACTICE PAGE

Chapter 23 Electric Current Series Circuits

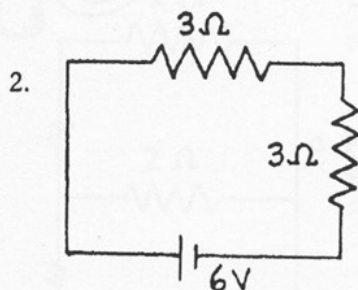1. In the circuit shown at the right, a voltage of 6 V pushes charge through a single resistor of $2\ \Omega$. According to Ohm's law, the current in the resistor (and therefore in the whole circuit) is _____ A.





THE EQUIVALENT RESISTANCE OF RESISTORS IN SERIES IS SIMPLY THEIR SUM!



If a second identical lamp is added, as on the left, the 6-V battery must push charge through a total resistance of _____ Ω . The current in the circuit is then _____ A.

3. The equivalent resistance of three $4\text{-}\Omega$ resistors in series is _____ Ω .
4. Does current flow *through* a resistor, or *across* a resistor? _____
Is voltage established *through* a resistor, or *across* a resistor? _____
5. Does current in the lamps occur simultaneously, or does charge flow first through one lamp, then the other, and finally the last in turn?

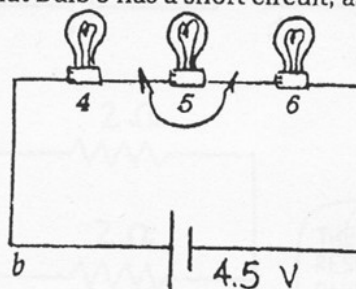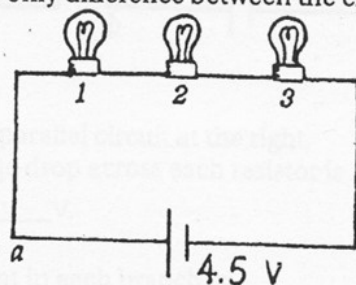6. Circuits *a* and *b* below are identical with all bulbs rated at equal wattage (therefore equal resistance). The only difference between the circuits is that Bulb 5 has a short circuit, as shown.




- In which circuit is the current greater? _____
- In which circuit are all three bulbs equally bright? _____
- What bulbs are the brightest? _____
- What bulb is the dimmest? _____
- What bulbs have the largest voltage drops across them? _____
- Which circuit dissipates more power? _____
- What circuit produces more light? _____

CONCEPTUAL *Physics* PRACTICE PAGE

Parallel Circuits

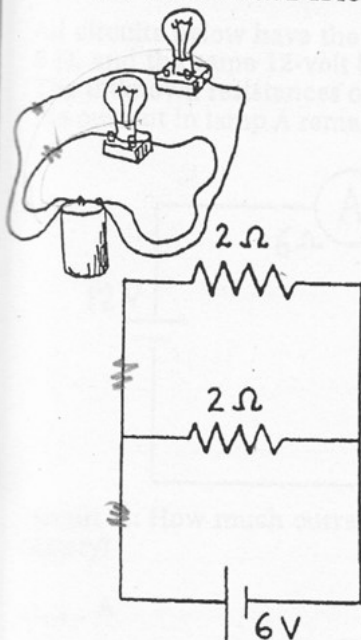1. In the circuit shown below, there is a voltage drop of 6 V across *each* 2- Ω resistor.




a. By Ohm's law, the current in *each* resistor is _____ A.





b. The current through the battery is the sum of the currents in the resistors, _____ A.

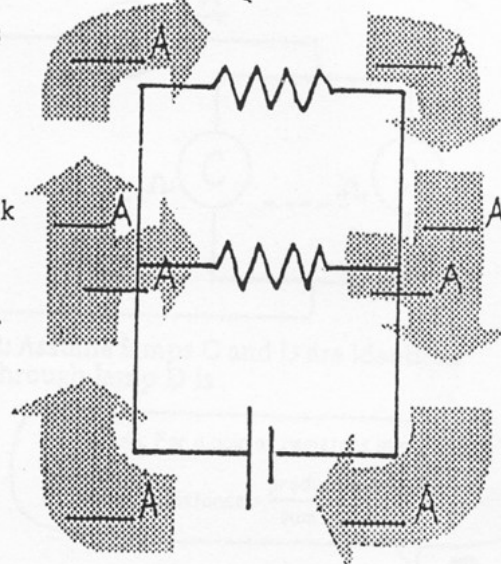c. Fill in the current in the eight blank spaces in the view of the *same* circuit shown again at the right.

THE SUM OF THE CURRENTS IN THE TWO BRANCH PATHS EQUALS THE CURRENT BEFORE IT DIVIDES.



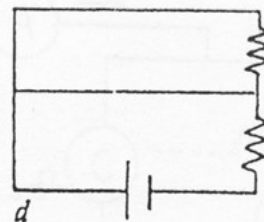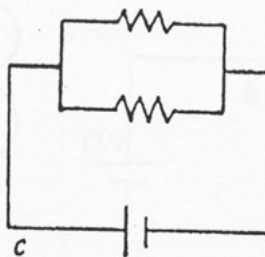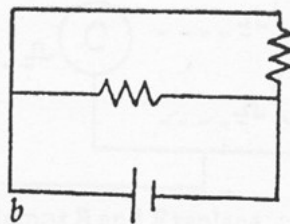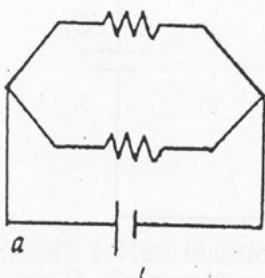2. Cross out the circuit below that is *not* equivalent to the circuit above.



3. Consider the parallel circuit at the right.

a. The voltage drop across each resistor is _____ V.

b. The current in each branch is:


2- Ω resistor _____ A

2- Ω resistor _____ A

1- Ω resistor _____ A

b. The current through the battery equals the sum of the currents which equals _____ A.

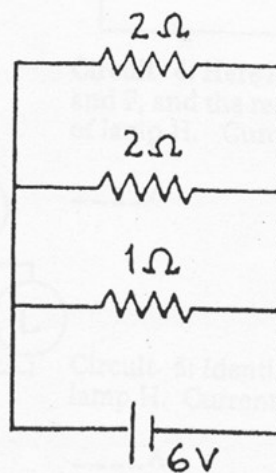c. The equivalent resistance of the circuit equals _____ Ω .



THE EQUIVALENT RESISTANCE OF A PAIR OF RESISTORS IN PARALLEL IS THEIR PRODUCT DIVIDED BY THEIR SUM!

